

Electric Power - Revisited

Lesson Notes

Learning Outcomes


- What are the mathematical equations for the power in electric circuits?
- How do you use those equations?

Electric Power - Review

Electric power refers to the rate at which work is done by the energy source upon the charge OR


... the rate at which energy is delivered to the load.

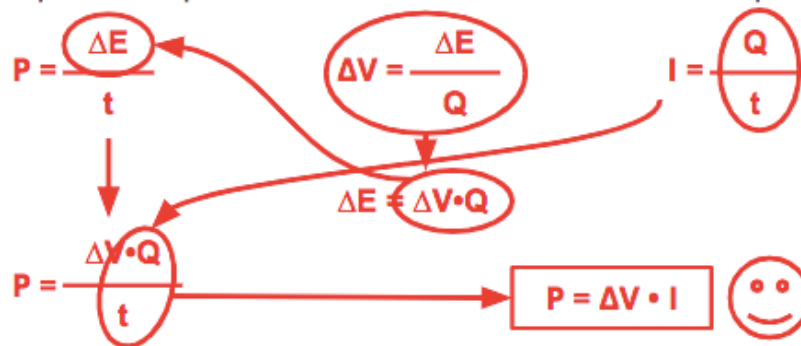An equation for power can be derived from these three equations.



Derivation of Power Equations

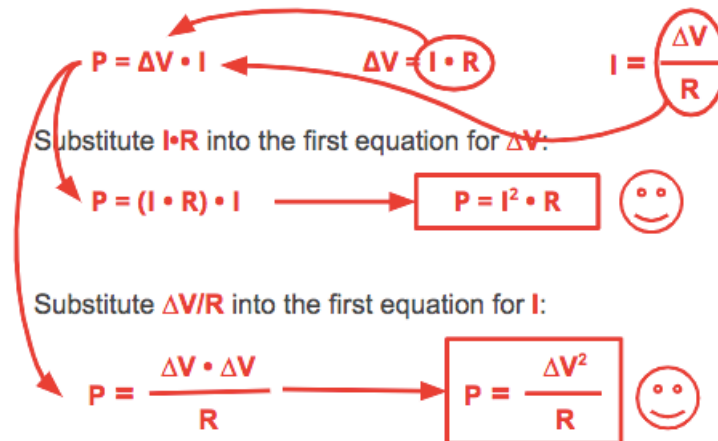Additional equations for power can be derived by combining ...



The Power Equations

We now have three equations for power. How and when does one use them?

Eq'n #1: $P = I \cdot \Delta V$

Eq'n #2: $P = I^2 \cdot R$

Eq'n #3: $P = \Delta V^2 / R$

These equations are often used in problems involving the computation of power (P) from known values of electric potential difference (ΔV), current (I), and resistance (R).

Known: $\Delta V, I \Rightarrow$ Use Equation 1

Known: $I, R \Rightarrow$ Use Equation 2

Known: $\Delta V, R \Rightarrow$ Use Equation 3

Think Conceptually!!!! (Always!!!)

When using ANY mathematical formula in Physics, it is important that you never divorce the concepts from the math.

Question: Compare the current of two bulbs - a 60-Watt bulb and a 120-Watt bulb - when placed in their own household circuit.

Wrong Path: Using $P = I^2 \cdot R$, the I^2 value for the 120-W bulb must be twice as much. Thus the I in the 120-W bulb is 1.41 X larger.

60-Watt Bulb:

$$P = \Delta V \cdot I$$

$$60 \text{ W} = (120 \text{ V}) \cdot I$$

$$I = (60) / (120) = \mathbf{0.50 \text{ A}}$$

120-Watt Bulb:

$$P = \Delta V \cdot I$$


$$120 \text{ W} = (120 \text{ V}) \cdot I$$

$$I = (120) / (120) = \mathbf{1.0 \text{ A}}$$

Answer: The 60-Watt bulb draws $\frac{1}{2}$ the current as the 120-Watt bulb.

Looking Deeper at 60-W vs. 120-W Bulbs

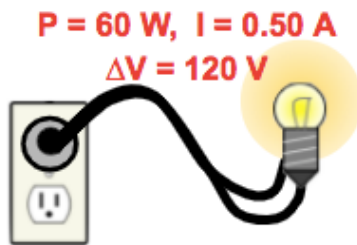Consider the 60-W and 120-W bulbs plugged into a 120-V outlet (US outlet).



$$P = 60 \text{ W}, I = 0.50 \text{ A}$$
$$\Delta V = 120 \text{ V}$$


$$R = \Delta V / I$$

$$R = (120 \text{ V}) / (0.50 \text{ A})$$

$$\mathbf{R = 240 \Omega}$$

$$P = \Delta V^2 / R = \mathbf{60 \text{ W}}$$
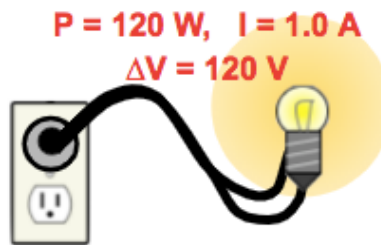
$$P = I^2 \cdot R = \mathbf{60 \text{ W}}$$



$$P = 120 \text{ W}, I = 1.0 \text{ A}$$
$$\Delta V = 120 \text{ V}$$

$$R = \Delta V / I$$

$$R = (120 \text{ V}) / (1.0 \text{ A})$$

$$\mathbf{R = 120 \Omega}$$

$$P = \Delta V^2 / R = \mathbf{120 \text{ W}}$$

$$P = I^2 \cdot R = \mathbf{120 \text{ W}}$$

$$P = \Delta V \cdot I$$
$$P = I^2 \cdot R$$
$$P = \frac{\Delta V^2}{R}$$