

### Still More Circuit Analysis

Read from Lesson 4 of the Current Electricity chapter at The Physics Classroom:


<http://www.physicsclassroom.com/Class/circuits/u914b.html>

<http://www.physicsclassroom.com/Class/circuits/u914c.html>

<http://www.physicsclassroom.com/Class/circuits/u914d.html>

MOP Connection: Electric Circuits: sublevel 11

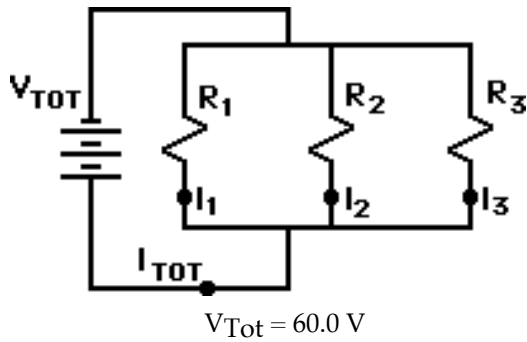1. Fill in the blanks in the following diagram. Show appropriate units.



$R_{Tot} =$  \_\_\_\_\_  $I_{Tot} =$  \_\_\_\_\_


$\Delta V_1 =$  \_\_\_\_\_  $I_1 =$  \_\_\_\_\_

$\Delta V_2 =$  \_\_\_\_\_  $I_2 =$  \_\_\_\_\_

$\Delta V_3 =$  \_\_\_\_\_  $I_3 =$  \_\_\_\_\_

$R_1 = 12.5 \Omega$      $R_2 = 14.7 \Omega$      $R_3 = 19.1 \Omega$

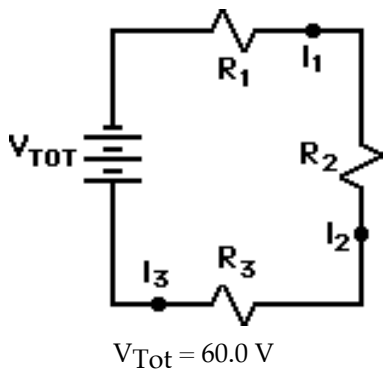2. Fill in the blanks in the following diagram. Show appropriate units.



$R_{Tot} =$  \_\_\_\_\_  $I_{Tot} =$  \_\_\_\_\_


$\Delta V_1 =$  \_\_\_\_\_  $I_1 =$  \_\_\_\_\_

$\Delta V_2 =$  \_\_\_\_\_  $I_2 =$  \_\_\_\_\_

$\Delta V_3 =$  \_\_\_\_\_  $I_3 =$  \_\_\_\_\_

$R_1 = 12.5 \Omega$      $R_2 = 14.7 \Omega$      $R_3 = 19.1 \Omega$

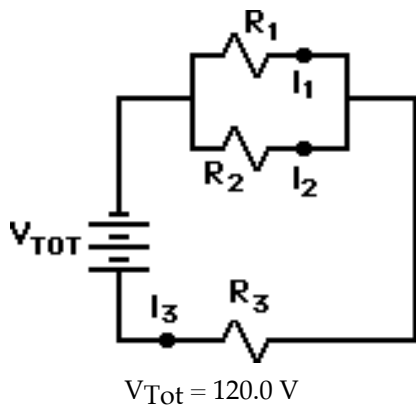3. Fill in the blanks in the following diagram. Show appropriate units.



$R_{Tot} =$  \_\_\_\_\_  $I_{Tot} =$  \_\_\_\_\_


$\Delta V_1 =$  \_\_\_\_\_  $I_1 =$  \_\_\_\_\_

$\Delta V_2 =$  \_\_\_\_\_  $I_2 =$  \_\_\_\_\_

$\Delta V_3 =$  \_\_\_\_\_  $I_3 =$  \_\_\_\_\_

$R_1 = 16.0 \Omega$      $R_2 = 16.0 \Omega$      $R_3 = 6.0 \Omega$

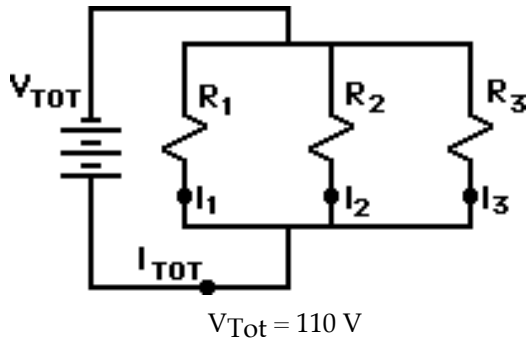4. Fill in the blanks in the following diagram. Show appropriate units.



$R_1 = 8.6 \Omega$       $R_2 = 5.4 \Omega$       $R_3 = 9.2 \Omega$


$R_{Tot} =$  \_\_\_\_\_      $I_{Tot} =$  \_\_\_\_\_

$\Delta V_1 =$  \_\_\_\_\_      $I_1 =$  \_\_\_\_\_

$\Delta V_2 =$  \_\_\_\_\_      $I_2 =$  \_\_\_\_\_

$\Delta V_3 =$  \_\_\_\_\_      $I_3 =$  \_\_\_\_\_

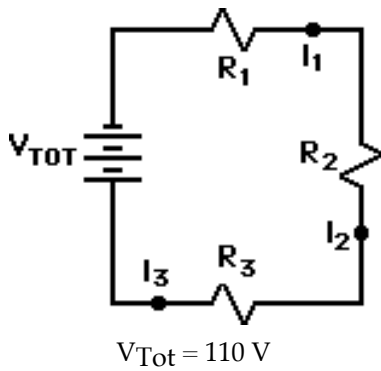5. Fill in the blanks in the following diagram. Show appropriate units.



$R_1 = 8.6 \Omega$       $R_2 = 5.4 \Omega$       $R_3 = 9.2 \Omega$


$R_{Tot} =$  \_\_\_\_\_      $I_{Tot} =$  \_\_\_\_\_

$\Delta V_1 =$  \_\_\_\_\_      $I_1 =$  \_\_\_\_\_

$\Delta V_2 =$  \_\_\_\_\_      $I_2 =$  \_\_\_\_\_

$\Delta V_3 =$  \_\_\_\_\_      $I_3 =$  \_\_\_\_\_

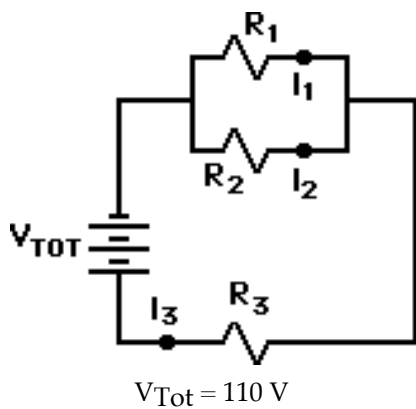6. Fill in the blanks in the following diagram. Show appropriate units.



$R_1 = 8.6 \Omega$       $R_2 = 5.4 \Omega$       $R_3 = 9.2 \Omega$

$R_{Tot} =$  \_\_\_\_\_      $I_{Tot} =$  \_\_\_\_\_

$\Delta V_1 =$  \_\_\_\_\_      $I_1 =$  \_\_\_\_\_

$\Delta V_2 =$  \_\_\_\_\_      $I_2 =$  \_\_\_\_\_

$\Delta V_3 =$  \_\_\_\_\_      $I_3 =$  \_\_\_\_\_